## Micro:bit Beverage Warmer for the Elderly

Component	Quantity	Photo						
Microbit	1	TEM-USE THE TOTAL SC THE TOT						
Edge Connector	1							
Relay	2							
Breadboard	1							


### **Major Electrical Components**

component	Quantity	energy and the second s
Fan	1	
12V Portable Car Battery Charger	1	
Heater	1	
TMP 36 (temperature sensor)	1	

#### **Major Electrical Components**

## Breadboard


# Holes highlighted in the same row/column are connected

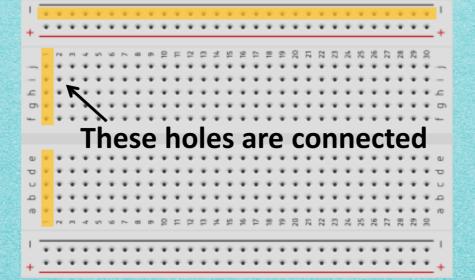


TMP36

#### We can use TMP 36 to measure temperature
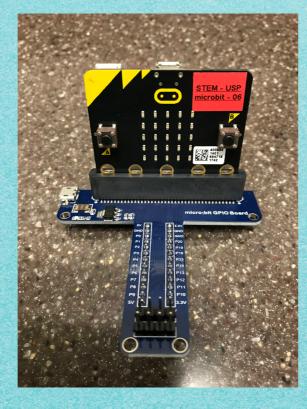
#### Step 1: insert microbit to edge connector


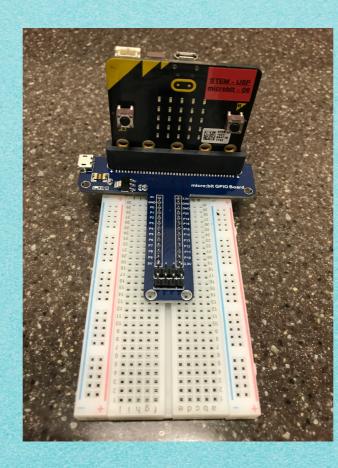
#### Step 2: Insert the edge connector to breadboard




Step 3: On the flat side of TMP 36, connect the following wires as shown

**Red -> left** 

**Blue -> middle** 

**Black -> right** 

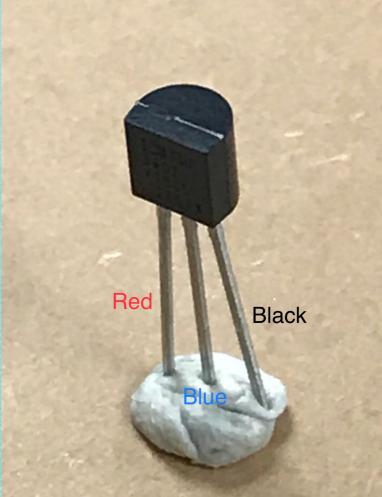


#### Step 4: Connect TMP 36 to edg follows: Red -> 5V

Blue -> pin o

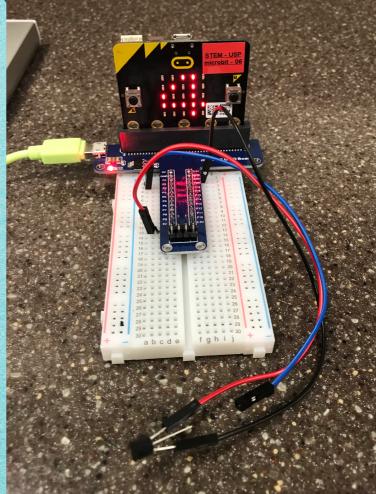
#### **Black -> GND**

Caution: TMP 36 will burn if the wires are not connected correctly


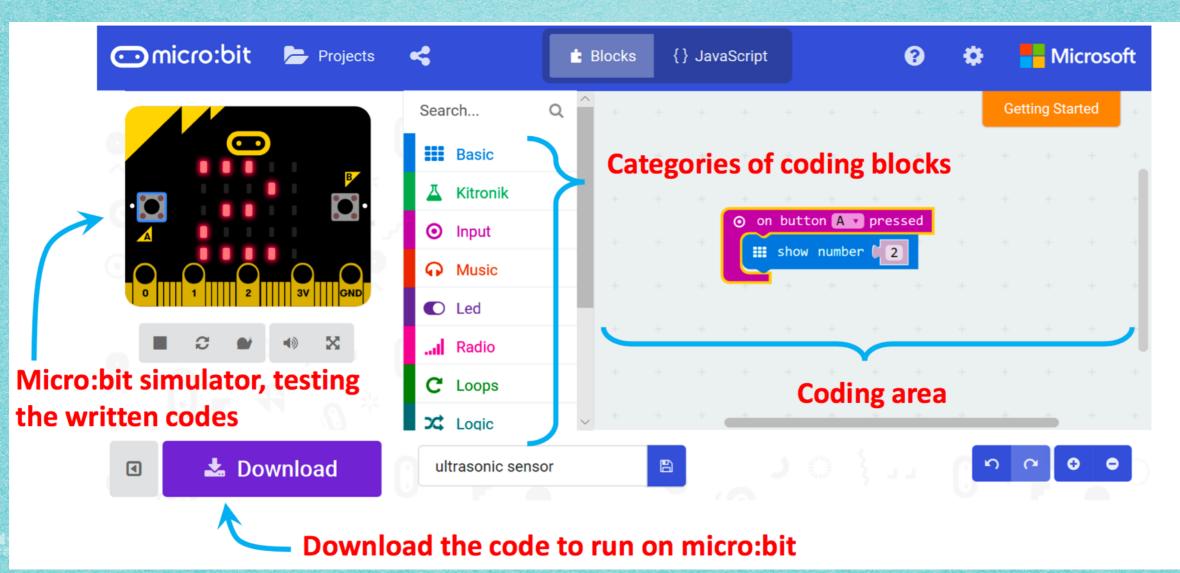
## Codes for Temperature Sensor (TMP 36)

go to http://microbit.org/code/, and choose **let's code**, we arrive at the coding area:



## Codes for Temperature Sensor (TMP 36)

#### Step 5: The following codes output the reading of

temperature senso Basic Construction Input

			4444444
- AND AND STATES AND	and a state of the second contract of the second of	while another and a same while while	while while the same while while while while

	Dasic
Inpu	t 🔪
Musi	с
Led	
Radio	
Loop	S
Logic	
Variabl	es
Math	
Adva	
Functio	ons
Arrays	
Text	
Gam	е
Image	S
Pins	

## Codes for Temperature Sensor (TMP 36)

Step 6: Calibrate the temperature sensor, and convert the readings of the sensor to temperature values in Celsius


forever							+								+
show number	round	•	ana	logı	read	pin	P0 🔻		× •	0.4	022	- •	77	2.777	
	+	+	+	+	+	+	+	+	+	+	+	+	+	+	+
+ + + +	+	+	+	+	+	+	+	+	+	+	+	+	+	+	+



High voltage devices could be controlled by Microbits using relays

Step 1: Connect wires to relay as shown

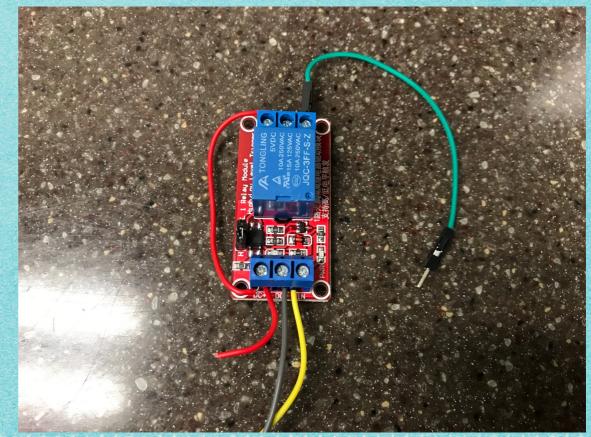DC+ -> COM, **red** wire DC- -> **grey** wire IN -> yellow wire NO -> **green** wire




## Control Fan with Relay

#### Step 2: Connect relay to breadboard as shown:

**Red -> 5V** 

Yellow -> pin 1

**Grey -> GND** 

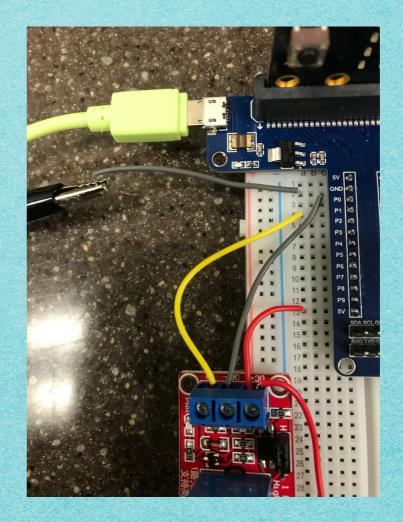


## Control Fan with Relay

#### Step 3: Connect relay to fan as shown:

#### **Green -> Fan**


#### **GND -> Fan**

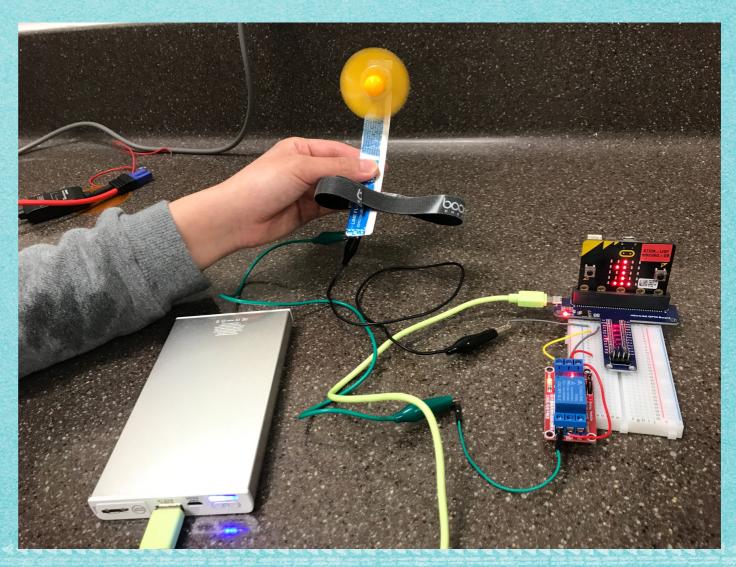

## Control Fan with Relay

#### Step 4: The following codes control the relay by pin 1

#### Check whether the fan works

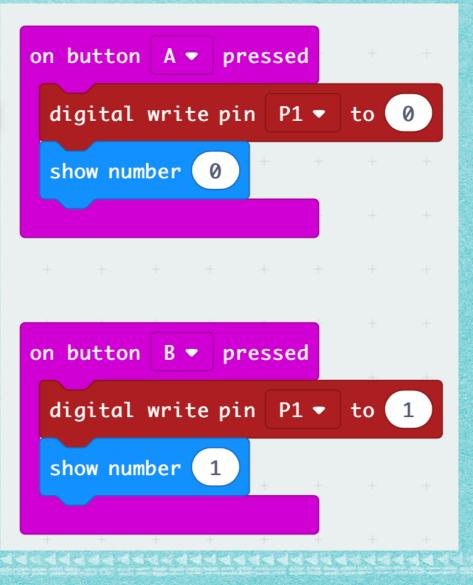


## Codes for Fan with Relay

#### To keep beverages at around 36 degree Celsius, Heater Off Fan **On** 38 36 35 34 37 **Temperature** (Celsius)

## Codes for Fan with Relay

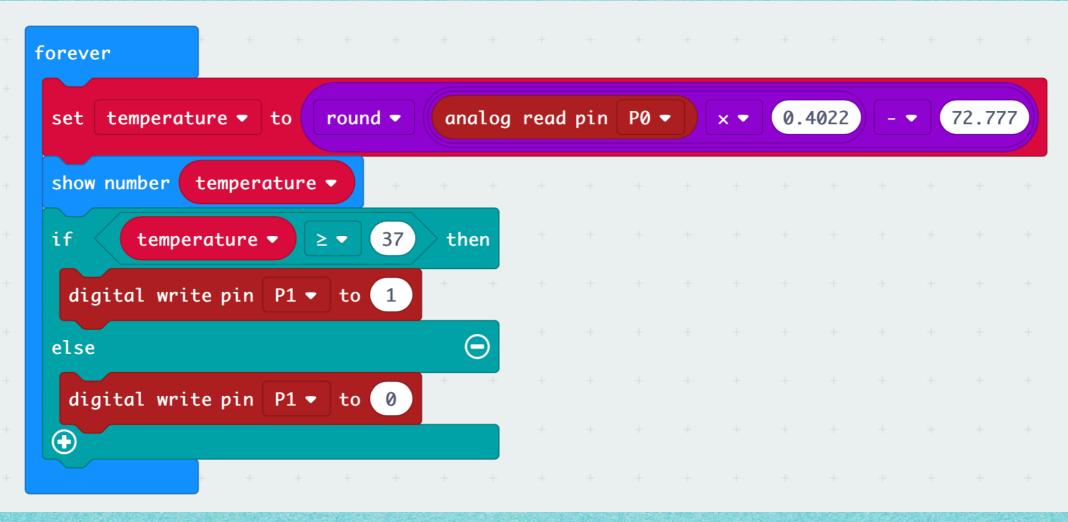
#### Step 5: The following codes switch on fan if temperature ≥37 degrees at pin 1



Step 1: Connect **12V Portable Car Battery Charger** to **breadboard** as shown


Red line on breadboard -> (+) of battery

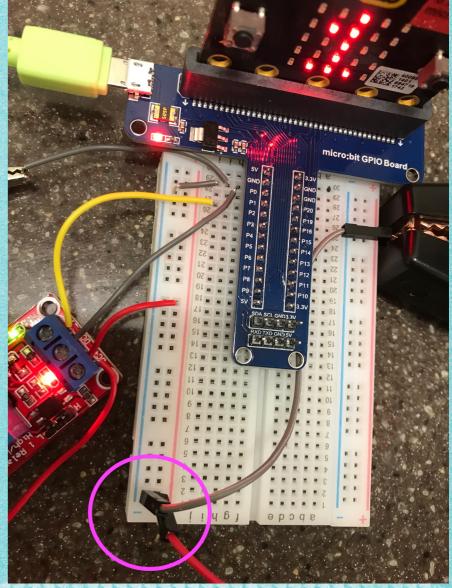Blue line on breadboard -> (-) of battery



#### Step 2: Connect common ground as shown

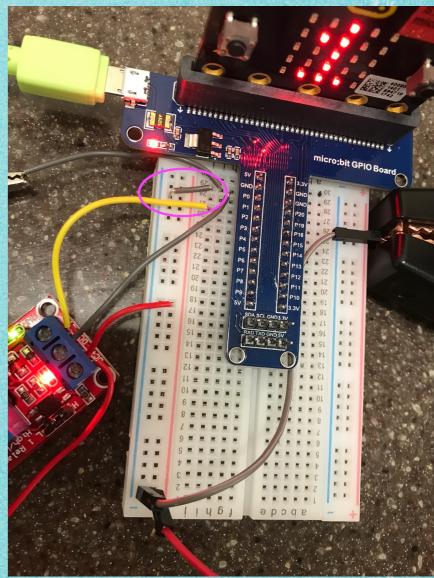
#### GND (edge connector) -> GND (blue line on breadboard)



#### Step 3: Connect relay to the breadboard Red -> 12V

Yellow -> pin 2


**Grey -> GND** 

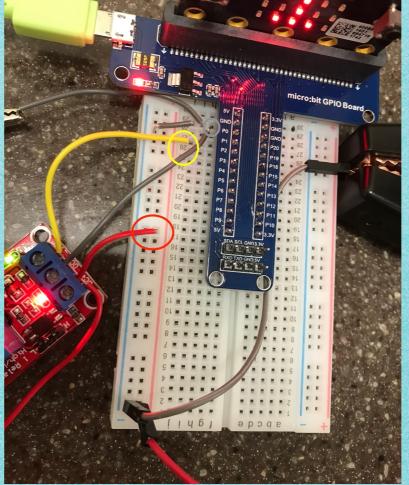

#### Step 3: Connect relay to heater as shown:


#### **Green -> Heater**

#### **GND -> Fan**

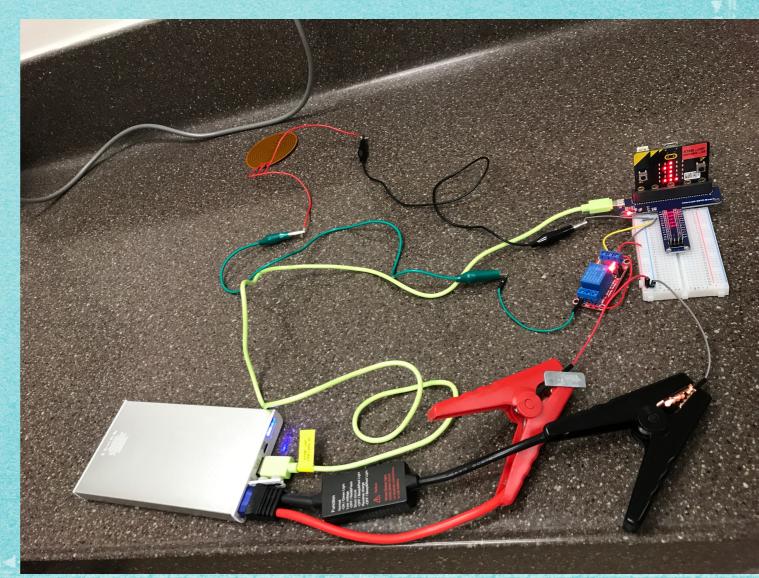

#### Step 4: The following codes control the relay by pin 2

#### Check whether the heater works

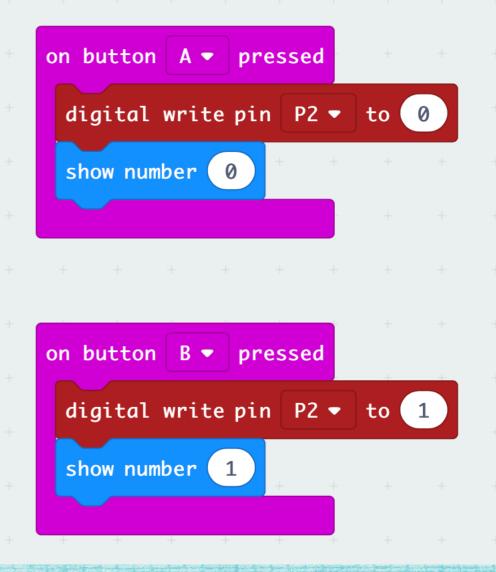

## Codes for Beverage Warmer


## To keep beverages at around 36 degree Celsius, Heater **On** Fan **Off**

34 35 36 37 38

#### **Temperature** (Celsius)

## Codes for Heater with Relay

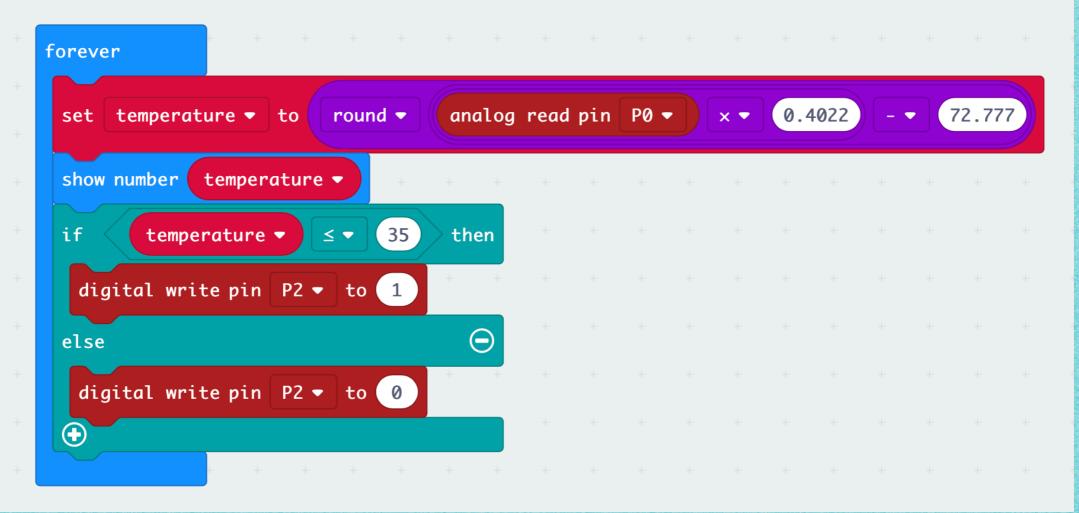
#### Step 5: The following codes switch on heater if temperature ≤ 35 degrees at pin 2



## Codes for Beverage Warmer

# Goal: keep beverages at around 36 degree CelsiusHeater On<br/>Fan OffHeater Off<br/>Fan OffHeater Off<br/>Fan On3435363738

## Codes for Beverage Warmer

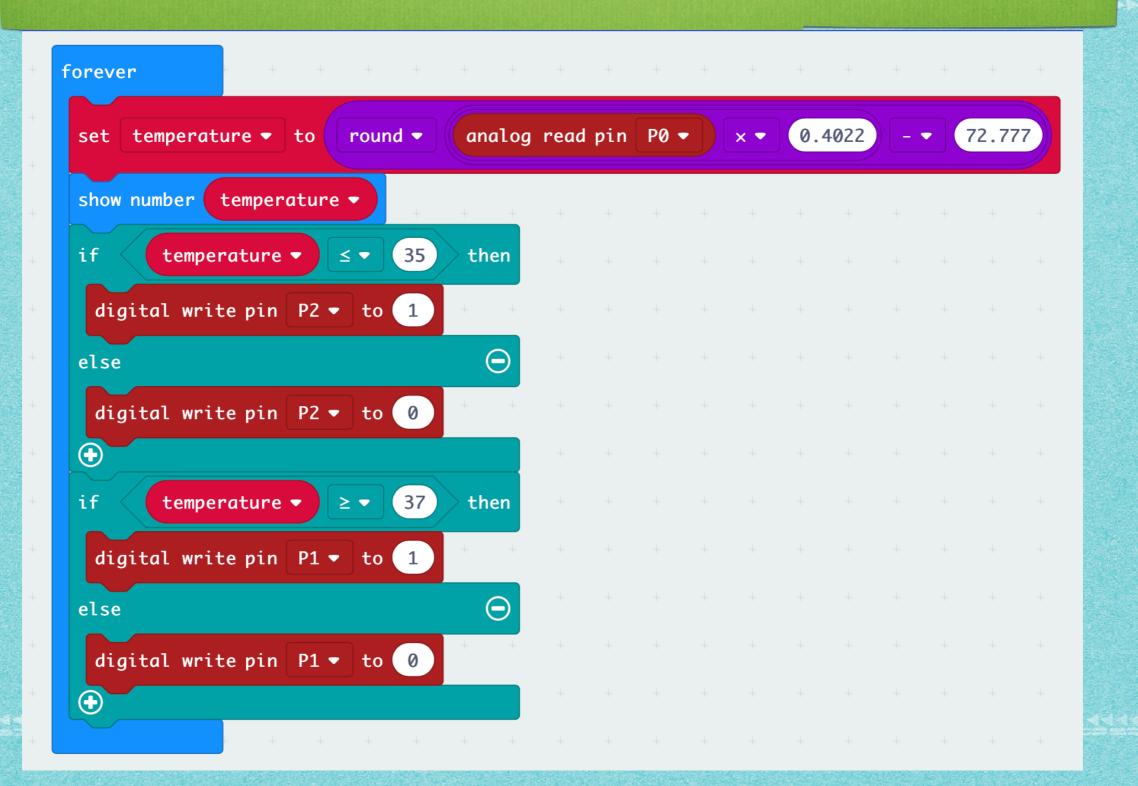

## Here is our Beverage Warmer

